 


LAB - 05


陳培殷老師 國立成功大學 資訊工程系



Introduction




■ 下載網址 - https://reurl.cc/eOQK7Q

 


■ 解壓縮後打開setup.bat




Next

 

■勾選選項

 

 ■ 完成後勾選Launch USB Blaster II driver installation



■ 跳出裝置驅動程式安裝精靈後一直按下一步




■ 出現"可以使用"就完成安裝了




Quartus II Tutorial (1/19)

 - Getting Started
 - Start the Quartus II software




Quartus II Tutorial (2/19)

 - Create a New Project
 - □ Open New Project Wizard (File → New Project Wizard...)




Quartus II Tutorial (3/19)

 Specify the working directory and the name of the project



Quartus II Tutorial (4/19)

 - Select "Empty project". Then, click "Next".
- Select design files. Or click "Next" to skip this step.




Quartus II Tutorial (5/19)

■ Specify device settings - (DE10-Lite Device family are used). Click "Next."


MAX 10(DA/DF/DC/SA/SC)

10M50DAF484C7G

 


Quartus II Tutorial (6/19)

 ■ Specify EDA Tool – (Modelsim-Altera is selected for simulation). Click "Finish."



Quartus II Tutorial (7/19)

 - Edit a new file by opening a Verilog HDL file
 - □ (File \rightarrow New \rightarrow Verilog HDL File \rightarrow OK)




Quartus II Tutorial (8/19)

Write Verilog code

Top module name 一定要跟 Project name 相同!!

輸入(input)		輸出(output)	
被加數(a)	加數(b)	和(sum)	進位(carry)
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 


```
module test (
input a,
input b,
output sum,
output carry
);

/* Write your code here. */
endmodule
```


Quartus II Tutorial (9/19)

 - Compiling the Designed Circuit (synthesis 合成)
 - **□** (Processing → Start Compilation)



Quartus II Tutorial (10/19)

Successful compilation

 



Quartus II Tutorial (11/19)

Edit a new file by opening a Verilog HDL file

□ (File \rightarrow New \rightarrow University Program VWF \rightarrow OK)


(vector waveform file)

 

 


Quartus II Simulation (12/19)

 - Simulating the Designed Circuit
 - Use node finder to find all the I/O pins (Edit → Insert → Insert Node or Bus…)




Quartus II Simulation (13/19)

 - Simulating the Designed Circuit
 - Selecting nodes to insert into the Waveform Editor




Quartus II Simulation (14/19)

 - Simulating the Designed Circuit
 - Selecting nodes to insert into the Waveform Editor




Quartus II Simulation (15/19)

 - Simulating the Designed Circuit
 - Select and edit waveform




Quartus II Simulation (16/19)

 - Simulating the Designed Circuit
 - Setting of test values




Quartus II Simulation (17/19)

 - Simulating the Designed Circuit
 - Run Functional Simulation




Quartus II Simulation (18/19)

 - Simulating the Designed Circuit
 - Save .vwf




Quartus II Simulation (19/19)

The result of functional simulation

 

Quartus II Simulation Notice


- 如果simulation時出現error,修改ModelSim-Altera路徑
 - □ 個人電腦: (Tools → Options → EDA Tool Options → ModelSim-Altera → C:\intelFPGA_lite\18.1\modelsim_ase\win32aloem)
 - □ 實驗室電腦: (Tools → Options → EDA Tool Options → ModelSim-Altera → C:\intelFPGA\16.1\modelsim_ase\win32aloem)

 



Lab I - Half Adder

a\b	0	1
0	0	1
1	1	0

$$sum=a \oplus b$$

 

 

 

Lab I - Half Adder

(a) Using Verilog to implement a 1-bit Half Adder

Please implement with 3 methods

- 1) Structural description
- 2) Data flow description
- 3) Behavioral description

(b) Simulation with waveform

Lab I - Hint


Structural Description

Verilog allows three kinds of descriptions for circuits:

(1) Structural description (2) Data flow description (3) Behavioral description

Structural description:


- module OR_AND_STRUCTURAL(IN,OUT);
- input [3:0] IN;
- output OUT;
- wire [1:0] TEMP;
- or u1(TEMP[0], IN[0], IN[1]);
- or u2(TEMP[1], IN[2], IN[3]);
- and (OUT, TEMP[0], TEMP[1]);
- 8. endmodule

 

Lab I - Hint

Data Flow Description

Data flow description

 

Lab I - Hint


Behavioral (RTL) Description

Behavioral description


```
    module OR_AND_BEHAVIORAL(IN, OUT);
```

```
2. input [3:0] IN;
```

- 3. output OUT;
- 4. reg OUT;
- 5. always @(IN)
- 6. begin
- 7. OUT = (IN[0] | IN[1]) & (IN[2] | IN[3]);
- 8. end
- 9. endmodule

 

Lab I - Simulation with waveform

 



a	b	sum	carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Lab II - Full Adder (1/2)

ab\c_in	0	1
00	0	1
01	1	0
11	0	1
10	1	0

ab\c_in	0	1
00	0	0
01	0	1
11	1	1
10	0	1

sum

=abc_in+abc_in+abc_in+abc_in

 $=(ab+ab)c_in+(ab+ab)c_in$

=(a⊕b)c_in+(a⊕b)c_in

=(a⊕b)⊕c_in

c_out


=ab+abc_in+abc_in

=ab+(ab+ab)c_in

 $=ab+(a\oplus b)c_in$

Lab II - Full Adder (2/2)

You can implement a full adder with (2 half adder and 1 or gate).

 

Lab II - Full Adder


(a) Using Verilog to implement a 1-bit Full Adder

Please implement with 3 methods

- 1) Structural description(with 2 half adder + 1 or gate)
- 2) Data flow description
- 3) Behavioral description

(b) Simulation with waveform

Lab II - Simulation with waveform

 

Notice

- 請勿在桌面建立 Project 及請勿命名中文資料夾
- Device family 請確認與 FPGA Chip 符合 (10M50DAF484C7G)
- Top module name & Project name 需要一致
- 確認 module ... endmodule 為keyword 變成藍色字體